



Jain College, Jayanagar
II PUC Mock Paper - I
Subject: Electronics

Duration: 3.15 minutes

Max.Marks: 100

PART-A

Answer all of the following

1x10=10

- 1) Why is FET called unipolar device?
- 2) Define Q point of a transistor.
- 3) Mention any one application of an open - loop OP-AMP.
- 4) Define skip zone.
- 5) What is the maximum deviation allowed in FM?
- 6) What is an antenna?
- 7) What is a don't care condition?
- 8) Define a full adder.
- 9) What is the capacity of internal ROM of 8051 microcontroller?
- 10) What is the operation performed by ! in c?

PART B

Answer any FIVE of the following.

2x5=10

- 11) What are the advantages of voltage divider bias circuit over other types of biasing methods?
- 12) Write any two characteristics of CB amplifier.
- 13) An amplifier has $Z_o=5K\Omega$, voltage gain $A=100$. If a negative feedback of $\beta=0.02$ is applied to it, what shall be the output impedance of the feedback amplifier?
- 14) Draw the circuit diagram of first order high pass filter.
- 15) Mention any two types of RC oscillators.
- 16) Explain the importance of i) accumulator ii) program counter in microcontroller.
- 17) Write the syntax of switch statement in c programming.
- 18) What is ISP? Mention its role in computer networking.

PART C

Answer any FIVE of the following.

- 19) Draw the drain characteristics of JFET. Explain different regions of drain characteristics.
- 20) Relate the bandwidth of an amplifier with and without feedback. Comment on the gain bandwidth product of an amplifier.
- 21) With necessary diagram explain virtual ground in Op-AMP.
- 22) With block diagram explain a wireless communication system.

- 23) Sketch modulating signal, carrier wave and AM wave.
- 24) Determine V_{dc} and I_{dc} of SCR FWR. Given firing angle is 60° , peak voltage of ac input to the rectifier is 325.2v and a load of 25Ω is connected.
- 25) Obtain the standard POS of $Y=(A+B).C$
- 26) List out any three additional features of 3G and 4G cell phone system.

PART D


Answer any **THREE** of the following

5x3=15


27) A CE amplifier using germanium transistor shown below, calculate

- i) Voltage drop across R_2
- ii) I_E
- iii) r_e^1
- iv) A_v
- v) A_i

given, $\beta=150$.

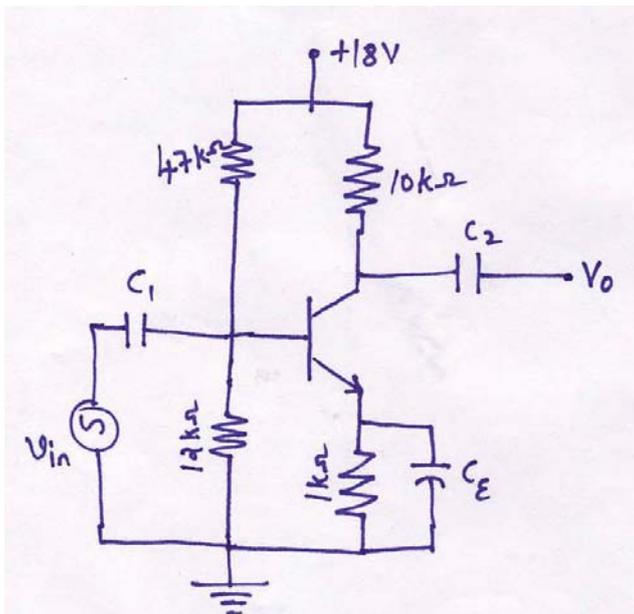

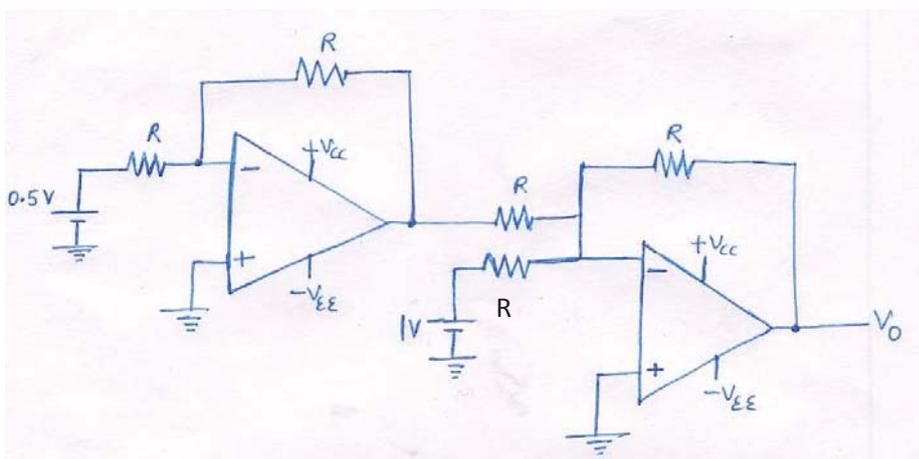28) Calculate the output voltage of the following OPAMP circuit.



- 29) In a colpitts oscillator, frequency of oscillation is 18MHz, Calculate the value of L to be used if $C_1 = 100\text{pF}$ and $C_2 = 10\text{pF}$.
Calculate the frequency of oscillation if C_2 is replaced by another capacitor of $C = 50\text{pF}$.
- 30) A 91.1MHz high frequency signal deviates to 91.16MHz while transmitting a signal of frequency 4KHz. Calculate the carrier swing, band width, percentage of modulation odulation in FM.
- 31) Simplify $Y = \sum m(4, 5, 7, 9, 11, 12, 13, 15) + \sum d(1, 3, 8)$ using K-Map. Draw the logic diagram for the simplified expression using only NAND gates.

PART E

Answer any four of the following.

(5X4 = 20)

- 32) With neat circuit diagram, explain the working and frequency response of direct coupled CE amplifier.
- 33) Derive an expression for the output of OPAMP subtractor
- 34) With neat block diagram, explain the AM transmitter system.
- 35) What is an Universal gate? Realize NOT, AND, OR and XNOR gates using NOR gate.
- 36) Write 8051 ALP to subtract 1Ah from 35h. Save the result in the RAM location 30h. Verify the content of 30h after executing the program.
- 37) Write a C program to check whether entered integer is even or odd. Print relevant statements.
