



**Jain College, Jayanagar**  
**II PUC Mock Paper - II**  
**Subject: Electronics**

**Duration: 3.15 minutes**

**Max.Marks: 100**

**PART – A**

**Answer all questions**

**1 X 10 = 10**

- 1) What is the function of drain in FET?
- 2) What is an active filter?
- 3) Define Signal to Noise ratio.
- 4) Expand SSB-SC
- 5) Which type of antenna is used in small electronic devices?
- 6) Name the circuit which converts fixed DC to variable DC.
- 7)  $10010111_{(BCD)} = \underline{\hspace{2cm}}_{(10)}$
- 8) Define combinational logic circuit.
- 9) Write an instruction to add content of R1 to the accumulator.
- 10) What are Identifiers?

**Part B**

**Answer any Five questions**

**2 X 5 = 10**

- 11) Write any two characteristics of CC Amplifier
- 12) An amplifier has  $Z_i = 5k\Omega$  and open loop voltage gain equal to 100,  $\beta=0.05$ . Find the output impedance after the application of negative feedback.
- 13) Sketch the output of an oscillator for
  - a.  $A\beta=1$
  - b.  $A\beta > 1$
- 14) A pn junction diode has a reverse saturation current rating of 50nA at 32°C. What should be the value of forward current for a forward voltage drop of 0.5V?
- 15) Sketch the input and output waveform of SCR-Half wave rectifier.
- 16) Mention any two addressing modes in microcontroller.
- 17) int a=5, b=25, c, d;
  - a. What is the value of b after the execution of  $b=++a$ ?
  - b. What is the value of C after the execution of  $c = b\%a$
- 18) Give any two advantages of wifi over Bluetooth.

## Part C

Answer any FIVE questions

3 X 5 = 15

- 19) Write any three difference between BJT and FET.
- 20) Explain the steps to obtain DC load line of voltage divider bias circuit.
- 21) Show how negative feedback affects bandwidth of an amplifier.
- 22) Write a note on sky wave propagation.
- 23) Explain
  - a. Selectivity
  - b. Sensitivity
  - c. Fidelity
- 24) Derive an expression for load voltage  $V_{dc}$  of an RC triggered SCR full wave rectifier.
- 25) What is a half subtractor? Draw the logic circuit using NAND gates. Mention the Boolean expression for outputs.
- 26) Explain the working of a transponder in satellite communication system with a neat block diagram.


## Part D

Answer any three questions:


5 X 3 = 15

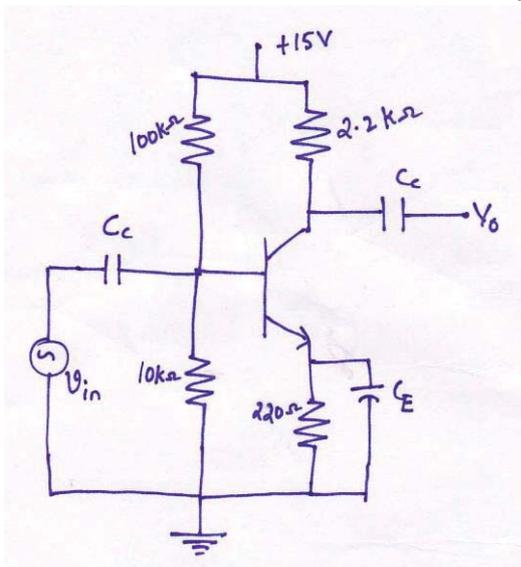- 27) For the CE amplifier circuit using silicon transistor given below, find
- i.  $A_v$
  - ii.  $A_p$
  - iii.  $Z_{in}$
  - iv.  $Z_o$

Given,  $I_E = 3.41\text{mA}$  and  $\beta = 100$ .



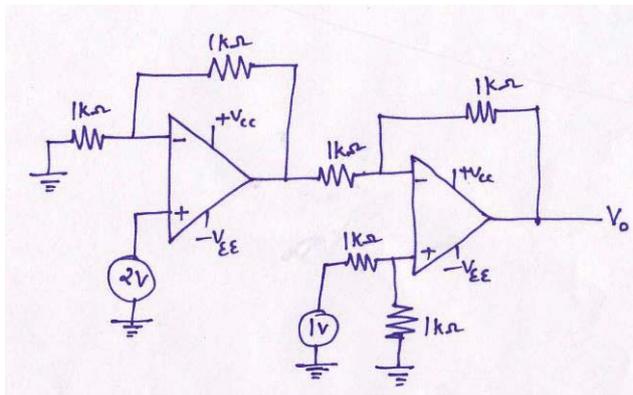28) Find the output voltage of the following circuit.



- 29) The frequency of a phase shift oscillator is 125KHz. If the value of capacitor used is  $0.22\mu\text{F}$ , calculate the value of resistance used. What will be the value of resistance if the capacitor is replaced by another capacitor of capacitance  $0.1\mu\text{F}$ .
- 30) A modulating signal  $10\sin 2\pi 10^3 t$  is used to amplitude modulate a carrier signal  $20\sin 2\pi 10^6 t$ . Find,
- $m_a$
  - Percentage of modulation
  - Frequencies of side bands.
  - Bandwidth
- 31) Simplify  $y = \sum m(0, 1, 4, 12, 15) + \sum d(2, 5, 7)$  using K-Map. Draw the logic diagram for the simplified expression using only NAND gates.

### Part E

Answer any FOUR of the following:

5 X 4 = 20

- With neat diagram, explain the working of class-B push-pull amplifier.
- Derive an expression for the output of an OPAMP integrator. Draw the output wave for sine wave input.
- Explain the working of an FM transmitter using block diagram.
- With neat logic diagram, explain the working of a master-slave JK flip flop. Write its Truth-table and draw timing diagram.
- Write 8051 ALP for adding 9Ah and 6Ch. Save the result in register R7. Verify the content of R7 and the status of carry flag after the execution of program.
- Write a C-program to find the sum of first n positive integers.

~\*~\*~