

SECOND PUC PREPARATORY EXAMINATION - 2020

Time : 3 Hrs. 15 Mins.

ELECTRONICS (40)

Max Marks : 70

No. of Pages : 02

Total No. of Ques. : 37

PART - A

I Answer all questions :

10x1=10

- 1) Name the terminals of FET.
- 2) Write the relation between I_{CEO} and I_{CBO} .
- 3) What is the value of output impedance of an ideal op-amp ?
- 4) Mention any two types of antennas.
- 5) Find excess-3 code for $(12)_{10}$.
- 6) Expand PBJT.
- 7) Which digital code is also called as unit-distance code ?
- 8) What is cell splitting ?
- 9) In which header file getch() and clrscr() functions are declared ?
- 10) Define Carrier Swing in FM.

PART - B

II Answer any FIVE questions :

5x2=10

- 11) Draw the frequency response of CE amplifier. Write formula for its Bandwidth.
- 12) Name the type of feedback used in amplifier and an oscillator.
- 13) An amplifier of gain 600 reduces to 50 after negative feedback. Calculate the feedback fraction.
- 14) State Barkhausen Criteria for sustained oscillations.
- 15) What is meant by a punch through p-n power diode.
- 16) Convert $AB + \bar{B}$ into canonical SOP expression.
- 17) State the different techniques used for improving capacity in cellular system.
- 18) Distinguish between uplink and downlink signals.

PART - C

III Answer any FIVE questions :

5x3=15

- 19) Write any three comparisons between BJT and FET.
- 20) Derive an expression for the DC load line for a transistor in CE mode biased with two sources.
- 21) Explain the different modes of propagation of electromagnetic waves.
- 22) With the graph, explain output characteristics of power transistor.
- 23) Sketch V-I characteristics of SCR for different gate currents and indicate their upon holding current, latching current and break over voltage.
- 24) What is data type ? How many types of data types are there in C.
- 25) Classify the instruction set of 8051 with respect to their functions.
- 26) Draw the block diagram of superheterodyne AM radio receiver. Sketch waveforms at different stages.

PART - D


I Answer any THREE questions :

3x5=15

27) The CE amplifier circuit using silicon transistor is given below calculate :

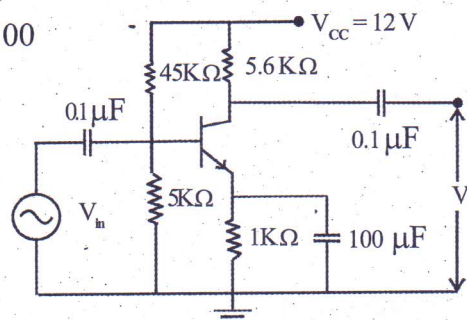
- i) Voltage across $5\text{K}\Omega$ ii) I_E iii) A_v iv) A_i v) A_p

Given $r_e^1 = \frac{26\text{mV}}{I_E}$, $\beta = 100$



(P.T.O)

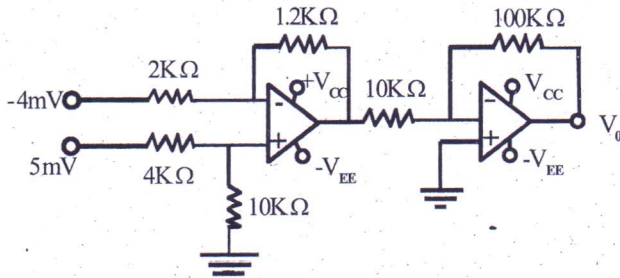28) Calculate the output voltage for the circuit shown below.



- 29) a) Determine the frequency of oscillations of Hartley Oscillator for the following values $L_1 = 3\text{mH}$, $L_2 = 5\text{mH}$ and $C = 10\text{nF}$
 b) Determine the frequency of oscillations and feedback ratio in a colpitts oscillator circuit containing the tank circuit with $L = 10\ \mu\text{F}$, $C_1 = 0.22\ \mu\text{F}$ and $C_2 = 0.47\ \mu\text{F}$.

30) A FM wave is represented by $V_{\text{FM}} = 10 \sin [2\pi \times 10^8 t + 5 \sin 2\pi \times 3 \times 10^3 t]$

Determine :

- Carrier frequency
 - Modulating signal frequency
 - Modulation index
 - Frequency deviation.
 - Carrier Swing.
- 31) Simplify the Boolean expression using K-Map.

$F(A, B, C, D) = \sum m(4, 5, 7, 9, 11, 12, 13, 15) + \sum d(1, 3, 8)$ using NAND gate draw the equivalent circuit to realize the simplified expression.

II Answer any four questions : 4x5=20

- With circuit diagram and input output waveforms, explain the working of two stage RC coupled amplifier.
- What is an op-amp integrator ? Draw the circuit of an Op-amp integrator and derive an expression for its output voltage.
- What is Amplitude modulation ? Derive an expression for instantaneous voltage of AM wave.
- Realise NOT, OR, AND and NAND gates using NOR gates.
- Write a C program to check a given number is even or odd.
- Write a program to add two 8-bit numbers and store it in R6. The numbers are 01EH and 01 CH.