




**PART-A**

**I Answer the following questions**

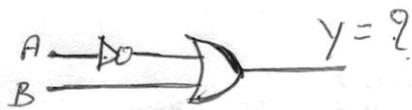**10 x 1 = 10**

- 1 What is the potential difference across a short circuit?
- 2 How many electrons are present in 1 C of charge?
- 3 What is the voltage across a fully charged capacitor of 10pF, when it is connected to a 10V supply?
- 4 Define time constant of RC circuit.
- 5 What is the majority charge carrier in p type material.
- 6 Draw the circuit diagram of series +ve clipper.
- 7 What is the function of emitter in a transistor?
- 8 In which mode of operation the transistor can be used as an amplifier.
- 9 What is the output of a four inputs OR gate if the inputs are A, 1, 0, and  $\bar{A}$ ?
- 10 Write the output expression.



**PART-B**

**II Answer only FIVE questions**

**5 x 2 = 10**


- 11 Mention any two applications of ECG.
- 12 Define spygniomano meter and glucometer.
- 13 Define time constant of a RC circuit and write the expression for the time constant.
- 14 Draw the lattice structure of p type SC.
- 15 Explain about photo transistor.
- 16 A transistor has an emitter current of 3mA and a collector current of 2.95mA. Calculate the base current.
- 17 Distinguish between the digital and analog signals.
- 18 Prove that  $A + \overline{AB} = A + B$ .

**PART-C**

**III Answer only FIVE questions**

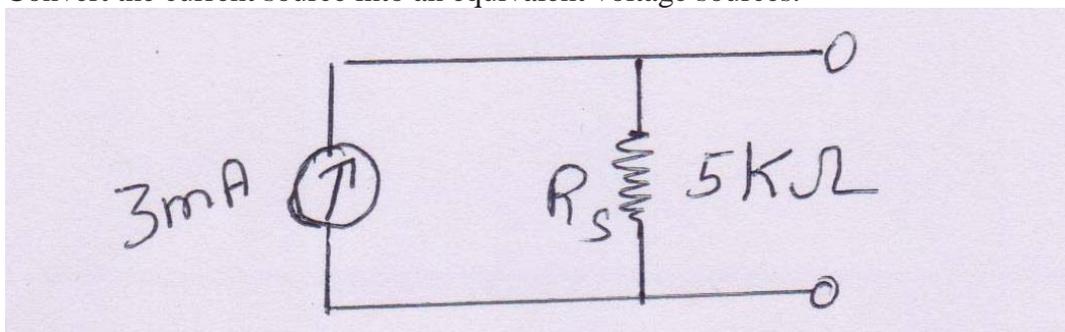**5 x 3 = 15**

- 19 a) Expand RADAR **1M**
- b) Mention any two applications of electronics in communication system. **2M**
- 20 Write any three properties of charge.
- 21 Convert the current source into an equivalent voltage sources.



- 22 Derive an expression for effective capacitance of two capacitors connected in series.
- 23 Write any three applications of LCD.
- 24 With a diagram briefly explain the formation of depletion region in the un biased semiconductor diode.
- 25 Explain double dabble methods with example.
- 26 Write the steps used in the PCB fabrication.

**PART-D**

**IV Answer any THREE for the following questions:**

**5 x 3 = 15**

- 27 An immersion coil dissipates 125w, when a voltage of 220v is applied. Calculate the numbers of charger flowing for every 2 sec.
- 28 a) Calculate effective capacitance between A and B (Given C = 10μF)



**2M**

- b) Determine the resistances of a copper wire of length 50 cm and diameter 2mm the resistivity of the wire  $1.72 \times 10^{-8} \Omega\text{m}$ . **3M**
- 29 A series circuit with  $R = 100\Omega$ ,  $L = 10\text{mH}$  and  $C = 10\mu\text{F}$  is connected to a 230V, 50 AC source calculate impedance, current flowing through circuit and phase angle.
- 30 For a zener diode voltage regulator with applied voltage of  $V_s = 10\text{V}$ , series resistor of  $R_s = 50 \text{ V}$ , Zener diode with zener voltage,  $V_z = 6\text{v}$  and load resistor  $R_L = 390\Omega$ . Determine: Load voltage, Voltage drop across series resistance, current through the zener diode and Minimum load resistance.
- 31 Subtract  $(111)_2$  from  $(1111)_2$  using 2's compliment continous method. Also verify the same by direct subtraction method.

**V Answer any FOUR questions:**

**5 x 4 = 20**

- 32 State and explain superposition theorem.
- 33 Explain the construction and working of moving coil loud speaker.
- 34 a) Explain about principle of transformer.  
b) Does a transformer work on DC?
- 35 a) Draw the series resonant (series LCR circuit) **1M**  
b) Find out the expression of impedance and resonant frequency of LCR circuit. **4M**
- 36 Explain the forward and reverse characteristics of a diode with neat circuit diagram and graph.
- 37 Explain diode AND gate with circuit diagram and Truth table.

\*\*\*\*\*